

**GURU NANAK INSTITUTE OF TECHNOLOGY**  
**An Autonomous Institute under MAKAUT**  
**2020-2021**  
**ANALOG ELECTRONIC CIRCUITS**  
**EI301**

**TIME ALLOTTED: 3 HOURS**

**FULL MARKS: 70**


*The figures in the margin indicate full marks.*  
*Candidates are required to give their answers in their own words as far as practicable*

**GROUP – A**  
**(Multiple Choice Type Questions)**

Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

		<b>Marks</b>	<b>CO No</b>
1.	(i) An ideal op-amp has CMRR and slew rate respectively a) infinity and infinity b) zero and infinity c) zero and zero d) infinity and zero.	1	CO1
	(ii) In an amplifier a coupling capacitor is used to a) Match the impedance b) Control frequency c) Limit bandwidth d) Prevent DC mixing with the output	1	CO1, CO2
	(iii) A differential amplifier is used at input stage of any operational amplifier to ensure a) High CMRR b) Wide Bandwidth c) High slew rate d) High open loop gain	1	CO1,CO3
	(iv) A V-I converter is a / an a) Transconductance amplifier b) Transresistance Amplifier c) Current Amplifier d) Operational Amplifier	1	CO1, CO2
	(v) Output pulse width for a monostable multivibrator using IC 555 where external resistance and capacitance are 20 KΩ and 0.1 μF is a) 2.1 s b) 2.2ms c) 2.5 s d) 2.2 μs	1	CO1,CO4

- |        |   |   |         |
|--------|---|---|---------|
| (vi)   | The gain required for the sustained oscillation in Wien Bridge oscillator is<br>a) 29<br>b) 1.5<br>c) 3<br>d) 1   | 1 | CO1,CO3 |
| (vii)  | A differential amplifier has the differential gain of 100, If its CMRR=240, then the common mode gain is<br>a) 0.24<br>b) 24000<br>c) 0.417<br>d) 1           | 1 | CO1,CO2 |
| (viii) | Schmitt trigger is also known as<br>a) squaring circuit<br>b) blocking oscillator<br>c) sweep circuit<br>d) astable multivibrator.                            | 1 | CO3     |
| (ix)   | For a wide range of oscillations in the audio range, the preferred oscillator is<br>a) Hartley<br>b) Phase shift<br>c) Wien bridge<br>d) Hartley and Colpitt. | 1 | CO2     |
| (x)    | In the figure below $v_1 = 8\text{ V}$ and $v_2 = 4\text{ V}$ . Which diode will conduct?   | 1 | CO2     |

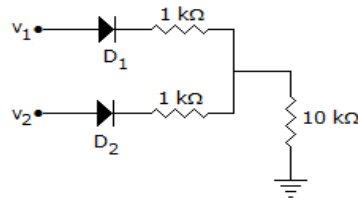

- |      |  |   |         |
|------|--|---|---------|
| (xi) | The voltage gain of an emitter follower circuit is<br>a) greater than 1<br>b) equal to 1<br>c) less than 1<br>d) none of these | 1 | CO1,CO3 |
|------|--|---|---------|


**GROUP – B**

**(Short Answer Type Questions)**

Answer any *three* from the following:  $3 \times 5 = 15$

			Marks	CO No
2.	(a)	Why a voltage divider bias circuit is known as self-bias circuit?	2	CO2

- |     |  |   |              |
|-----|--|---|--------------|
| (b) | A silicon transistor with $\beta = 50$ , $V_{BE} = 0.6V$ , $V_{CC} = 22.5 V$ and $R_C = 5.6 K$ is used for self-biasing circuit. It is desired to establish a Q point at $V_{CE} = 12 V$ . $I_C = 1.5 mA$ and stability factor $S \leq 3$ . Find $R_E$ , $R_1$ and $R_2$ ( The symbols have their usual meanings).     | 3 | CO2,CO4      |
| 3.  | (a) Explain how the bandwidth of an amplifier will be increased using negative feedback  | 2 | CO1,CO2, CO3 |
|     | (b) Prove that the gain of the amplifier used in a Wien bridge oscillator must be greater than 3 for sustained oscillations  | 3 | CO1,CO2, CO3 |
| 4.  | (a) Why a voltage divider bias circuit is known as self-bias circuit?  | 2 | CO2,CO3      |
|     | (b) A silicon transistor with $\beta = 50$ , $V_{BE} = 0.6V$ , $V_{CC} = 22.5 V$ and $R_C = 5.6 K$ is used for self-biasing circuit. It is desired to establish a Q point at $V_{CE} = 12 V$ . $I_C = 1.5 mA$ and stability factor $S \leq 3$ . Find $R_E$ , $R_1$ and $R_2$ ( The symbols have their usual meanings). | 3 | CO2,CO3      |
| 5.  | (a) For the following circuit find the output voltage using the data given as following.   | 5 | CO1,CO4      |

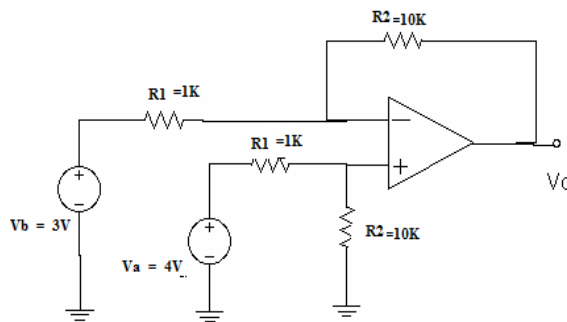


- |    |   |   |     |
|----|---|---|-----|
| 6. | (a) Find out the condition of an astable multivibrator so that its duty cycle would be less than 50% and draw the circuit diagram | 5 | CO3 |
|----|---|---|-----|

**GROUP – C**  
**(Long Answer Type Questions)**

Answer any *three* from the following: **3×15=45**

- |    |   | <b>Marks</b> | <b>CO No</b> |
|----|---|--------------|--------------|
| 7. | (a) Explain how it is possible to achieve better Q-point stabilization by using self-bias circuit.  | 4            | CO2,CO3      |
|    | (b) Consider a self bias circuit with an npn silicon transistor CE configuration. The circuit is designed in such a way that the $I_C = 1.5 mA$ , $V_{CE} = 10 V$ and the stability factor is less than equal to 6. If $V_{CC} = 20V$ , $V_{BE} = 0.7 V$ , $B = 100$ , $R_C = 5K$ , calculate the values of $R_E$ , $R_1$ , $R_2$ | 7            | CO2,CO3      |
|    | (c) How the operating point of a transistor can shift ? How will you define the stability factors for a transistor ?  | 4            | CO2,CO3      |
| 8. | (a) What is free running oscillator? Derive the expression for time period.   | 4            | CO2,CO3      |

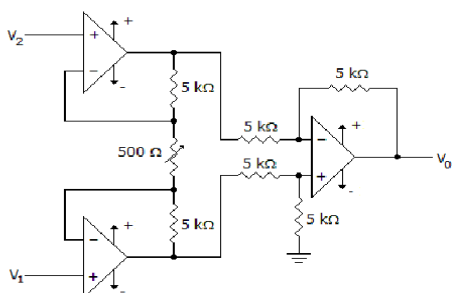- |     |     |   |    |         |
|-----|-----|---|----|---------|
|     | (b) | How can the duty cycle be 50% by adding diode?  | 4  | CO2,CO3 |
|     | (c) | For a astable multi-vibrator using 555 timer $R_A = 6.8 K$ ,<br>$R_B = 3.3 K$ and $C = 0.1 F$ , calculate (i) $t_{HIGH}$<br>(ii) $t_{LOW}$ (iii) free running frequency (iv) duty cycle,  | 7  | CO2,CO3 |
| 9.  | (a) |    | 5  | CO1,CO4 |
|     |     | Calculate the output voltage for $V_1=5V$ and $V_2=2.5V$  |    |         |
|     | (b) | Draw the output waveforms if input of a differentiator is<br>i) Triangular wave<br>ii) Square wave  | 5  | CO2,CO4 |
|     | (c) | Explain the monostable operation of NE555 with proper circuit diagram and waveform.   | 5  | CO2,CO4 |
| 10. | (a) | What is crossover distortion in Class B amplifier and how can it be removed.  | 4  | CO3     |
|     | (b) | Draw the h-parameter equivalent circuit of low frequency CE mode transistor amplifier and hence calculate the current gain , Voltage gain,I/P impedance & O/P impedance in terms of h-parameters  | 7  | CO2,CO3 |
|     | (c) | With a proper circuit diagram, explain the operation of phase shift oscillator circuit.   | 4  | CO4     |
| 11. | (a) | Design Schmitt trigger circuit using Op-amp which has a maximum output voltage +10V and -10V.The hysteresis $V_H$ should be 0.4V.Explain the working of the circuit with the transfer characteristics .Use a reference voltage $V_R=2V$ | 10 | CO2,CO4 |
|     | (b) | With reference to Schmitt Trigger using Op-Amp,define UTP and LTP,Explain why hysteresis is introduced in Schmitt Trigger   | 5  | CO2,CO4 |