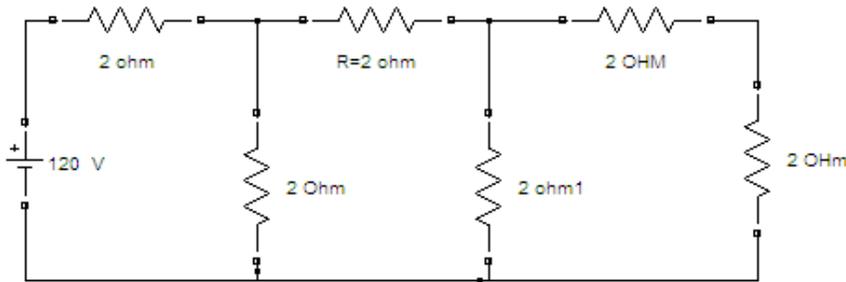


- 1(xi) A low pass filter passes _____ frequencies 1 CO 1
 a) a band of b) lower
 c) higher d) All the frequencies
- 1(xii) Laplace transform of Impulse signal is 1 CO 3
 a) $1/S$ b) $1/S^2$
 c) 1 d) S

GROUP – B
 (Short Answer Type Questions)
 (Answer any *three* of the following)


3 x 5 = 15
Marks **CO No**
 5 **CO 1**

2. Calculate the power dissipated in the resistor R




3. a) State & prove the Maximum Power transfer theorem. 5 CO 1
 b) Show the efficiency for maximum power transfer theorem is 50%.

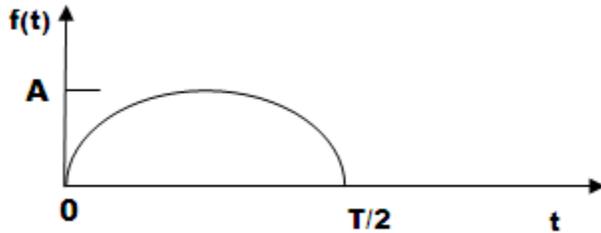4. Determine the Laplace Transform of the given signal 5 CO 2



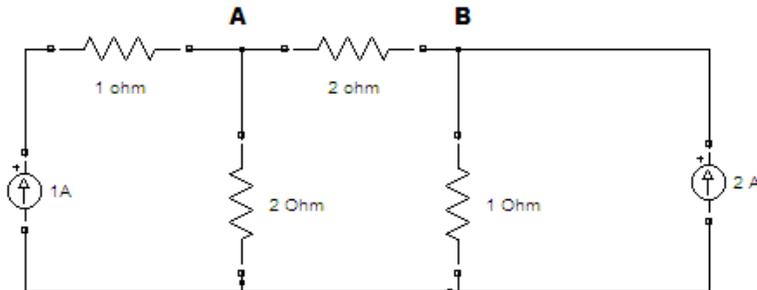
5. Determine the voltage V_{AB} of figure by node analysis 5 CO 1



6. State Superposition Theorem. Using this theorem calculate the current through the R of the circuit shown in the figure below.

5


CO 1

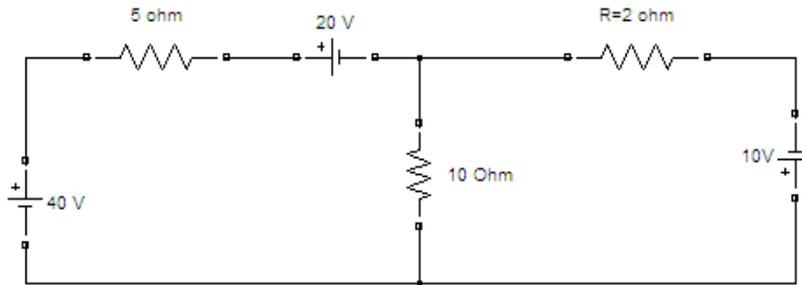

GROUP – C
(Long Answer Type Questions)
 (Answer any *three* of the following)

3 x 15 = 45
Marks CO No
 5 CO 1

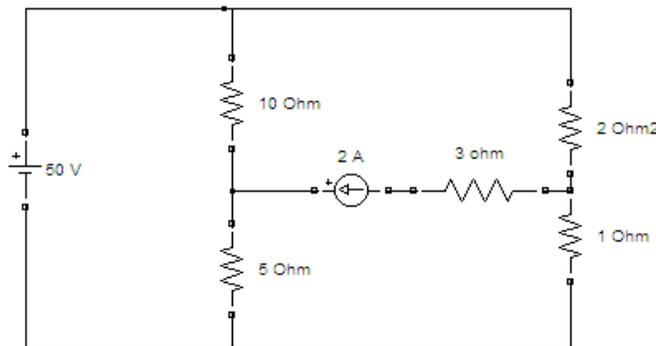
7. a) Find out the loop currents using super mesh analysis.



7. b) State Superposition Theorem. Using this theorem calculate the current through the R of the circuit shown in the figure below..

5


CO 1

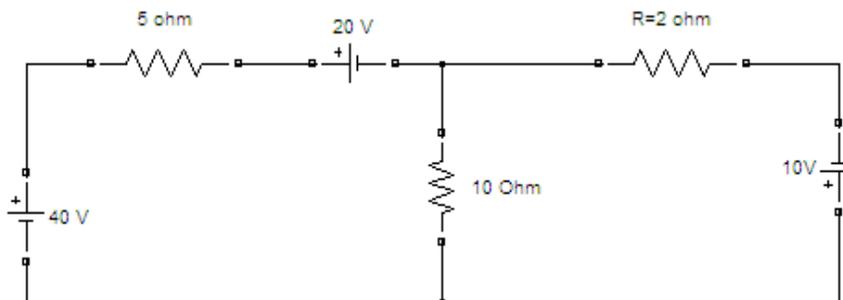

7. c) Find the voltage across the Resistance R.

5

CO 1

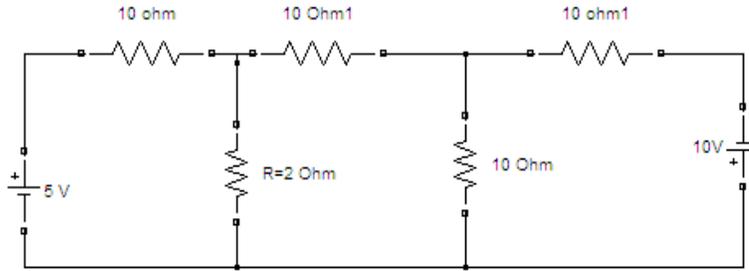

8.a) State & prove Final value theorem.


4

CO 1

8.b) What should be the value of impedance R for maximum power to be transferred from the sources. Obtain the amount of maximum power.

6


CO 1

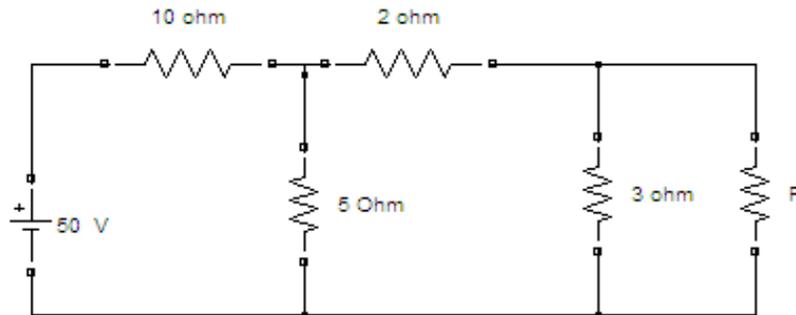


8.c) Determine current through the resistance R using Millman's theorem.

5


CO 1

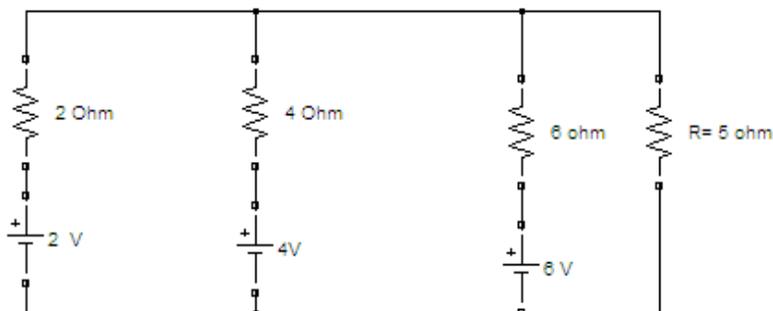

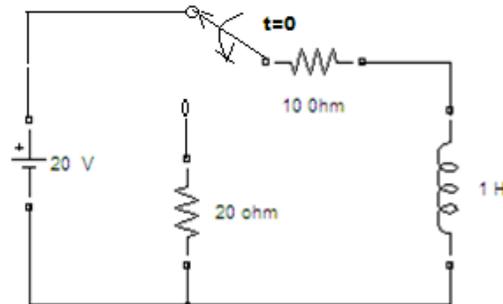
- 9.a) The circuit given initially at steady state with switch at position 'a'. If the switch position is changed from a to b at time $t=0$, find the current after switching. 5 CO 2



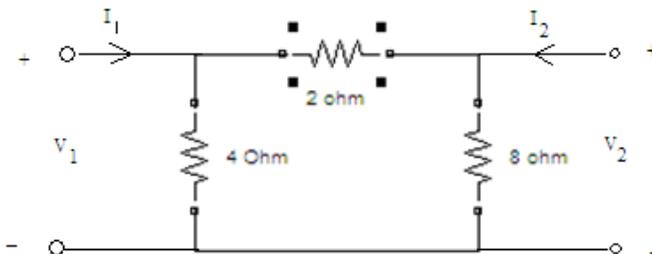- 9.b) Find the transient response of R-L series circuit due to step input signal. 5 CO 2
- 9.c) Design a band pass filter with $f_L=200$ Hz & $f_H=1$ KHz and a pass band gain=4. Also calculate Q of the filter. 5 CO 5
10. a) Determine for a two port network the condition of reciprocity and condition of symmetry in terms of Z parameter. 5 CO 4
10. b) Define ABCD parameters of a two port network. Where are they most efficiently used? 4+1 CO 4
10. c) Find the Y parameters of the following circuit. 5 CO 4



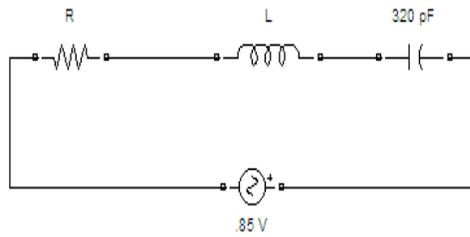- 11.a) For the circuit shown in figure determine the value of inductance for resonance if $Q=50$ and $f_0=175$ kHz. Also find the circuit current and the band-width of the circuit. 6 CO 5



- 11.b) What is selectivity of a resonant circuit? prove that the selectivity is the quality factor. 4 CO 3
- 11.c) a) Prove that resonance frequency $f_0 = 1/2\pi\sqrt{LC}$ for a R-L-C series network. 2+3 CO 3
- b) For a R-L-C network, prove bandwidth is the ratio of resonance frequency to the quality factor