

**GURU NANAK INSTITUTE OF TECHNOLOGY**  
**An Autonomous Institute under MAKAUT**  
**2020-2021**  
**CIRCUIT THEORY AND NETWORK**  
**CS303**

**TIME ALLOTTED: 3 Hours**

**FULL MARKS: 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP – A**

**(Multiple Choice Type Questions)**

Answer any *ten* from the following, choosing the correct alternative of each question: **10×1=10**

	<b>Marks</b>	<b>CO No</b>
1(i) The system $y(t) = tx(t) + 4$ is a) non linear, time varying and unstable b) linear, time varying and unstable c) non linear, time- invariant and unstable d) non linear, time varying and stable	1	CO3
1(ii) The theorem that enables a number of voltage (or current) sources to be combined directly into a single voltage (or current) source is the .....theorem a) Superposition b) Reciprocity c) Milliman's d) . Thevenin	1	CO1
1(iii) A R-L series circuit has a time constant given by a) R/L b) L/R c) 1/(RL) d) 2RL	1	CO3
1(iv) Laplace transform of $\sin(at)u(t)$ is? a) $s / a^2 + s^2$ b) $a / a^2 + s^2$ c) $s^2 / a^2 + s^2$ d) $a^2 / a^2 + s^2$	1	CO2
1(v) How is the discrete time impulse function defined in terms of the step function? a) $d[n] = u[n+1] - u[n]$ b) $d[n] = u[n] - u[n-1]$ c) $d[n] = u[n] - u[n-2]$ d) $d[n] = u[n+1] - u[n-1]$	1	CO2
1(vi) When a unit impulse voltage is applied to an inductor of 1H, the energy supplied by the source is a) Infinite b) 0 c) 1/2J d) 1J	1	CO1

- |         |  |   |     |
|---------|--|---|-----|
| 1(vii)  | The no of links for a graph having n nodes and b branches are<br>a) $b-n+1$<br>b) $n-b+1$<br>c) $b+n-1$<br>d) $b+n$  | 1 | CO5 |
| 1(viii) | A tie set matrix has 3 rows and 7 branches. The number of twigs is<br>a) 3<br>b) 5<br>c) 2<br>d) 4   | 1 | CO5 |
| 1(ix)   | A two port network is symmetrical if and only if<br>a) $Z_{11}=Z_{22}$<br>b) $BC-AD= -1$<br>c) $A=D$<br>d) $Y_{11}=Y_{21}$   | 1 | CO4 |
| 1(x)    | Under the condition of maximum power transformation, efficiency of the circuit is<br>a) 100%<br>b) 50%<br>c) 25%<br>d) 75%   | 1 | CO1 |
| 1(xi)   | The coefficient of coupling for two coils having $L_1=2H$ , $L_2=8H$ , $M= 3H$ is<br>a) 0.75<br>b) 0.1875<br>c) 1.333<br>d) 5.333  | 1 | CO1 |
| 1(xii)  | The input and output of a continuous time system are respectively denoted by $x(t)$ and $y(t)$ , which of the following description corresponds to a causal system?<br>a) $y(t)= x(t-2)+x(t-4)$<br>b) $y(t)=x(t-4)x(t+1)$<br>c) $y(t)=x(t+4)x(t-1)$<br>d) $y(t)=(t+5)x(t+5)$ | 1 | CO3 |


**GROUP – B**

**(Short Answer Type Questions)**

(Answer any *three* of the following)


**3 x 5 = 15**  
Marks    CO No  
5        CO1

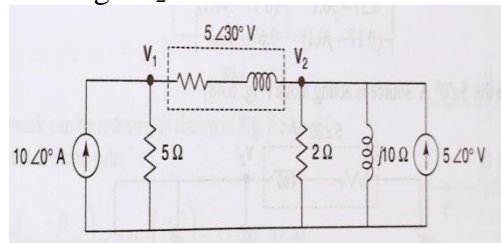2. Find the node voltage  $V_2$  in the network of the following Figure.




- |      |   |   |     |
|------|---|---|-----|
| 3.b) | Explain the concept of mutual inductance with a suitable example.                                   | 2 | CO1 |
| 3.b) | Derive the expression between self-inductances of two coils and the mutual inductance between them. | 3 | CO1 |

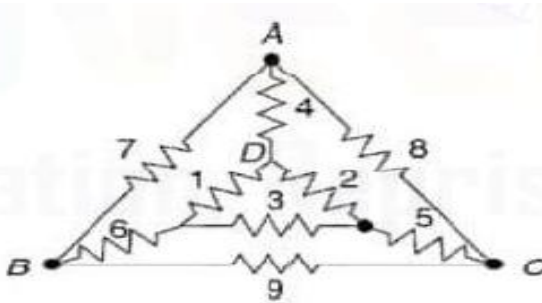- 4 Find a tree from the graph of the network shown in the below figure. 5 CO5  
 Make the tie-set matrix and write the equations loop currents. All the values given in the figure are in ohms.



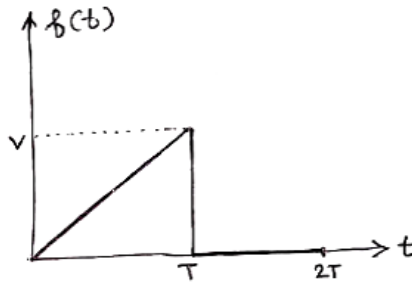- 5 Find the laplace transform of the waveform shown in figure. 5 CO3



- 6 A Series resonant circuit has an impedance of 500 ohm at resonant frequency. Cut off frequencies are 10 kHz and 100 Hz. Determine (a) resonant frequency (b) value of L, C, and (c) quality factor at resonant frequency. 5 CO3


**GROUP – C**

**(Long Answer Type Questions)**


(Answer any *three* of the following)

**3 x 15 = 45**  
 Marks CO No  
 5 CO3

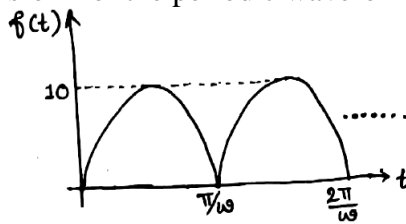
- 7.a) Find the laplace transform of the periodic waveform shown in figure.



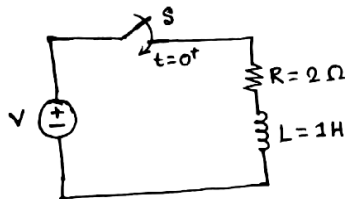
- 7.b) For an RL series circuit shown in figure, with no initial current in the inductor, a voltage  $V = 4e^{-t}$  volts is applied at  $t = 0$  sec. find the expression for the resulting current in the circuit for  $t \geq 0$  using laplace transform method. 5 CO2



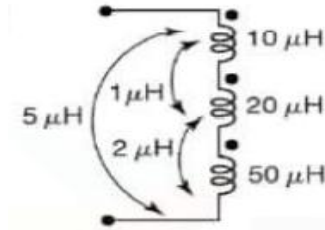
- 7.c) Find the inverse Laplace transform of  $F(s) = \frac{s^2 - 15s - 11}{(s+1)(s-2)^2}$  5 CO2
- 8.a) What are the conditions for system to be a linear system? Give one practical example each of an ideal voltage source and ideal current source. 5 CO3
- 8.b) Find the effective value of the inductance for the following connection 5 CO1



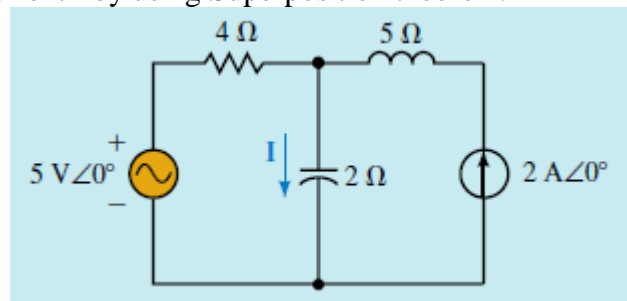
- 8.c) Prove,  $k = \frac{M}{\sqrt{L_1 L_2}}$ , Where k= coupling co-efficient, M= Mutual inductance and  $L_1 L_2$  are the self inductance of a coupled circuit. 5 CO1
- 9.a) State and explain Norton theorem. 6 CO1
- 9.b) Find the current I by using Superposition theorem. 9 CO1



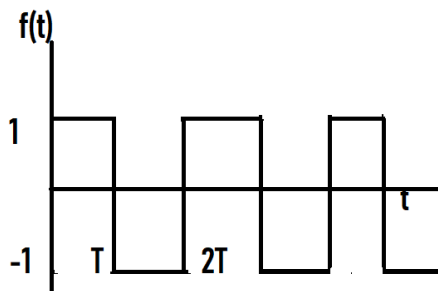- 10.a) A capacitor of 5 micro Farad is charged initially to 10V and connected to 10KOhm resistance. It is allowe to discharge through it by witching of a switch k. find the discharging current. 5 Co2
- 10.b) Obtain the Laplace transform of the given square wave train. 6 Co2



- 10.c) 4 Co2

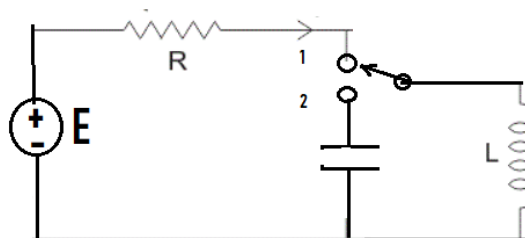

- Obtain expression for current flowing through the circuit.
- 11.a) Define incident matrix of a graph and draw the orientation graph from the reduced incident matrix. 6 CO5

$$[A] = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

11.b) For the network shown in figure obtain current ,I through 8 V battery.

9 CO5

