

GURU NANAK INSTITUTE OF TECHNOLOGY

An Autonomous Institute under MAKAUT

2020-2021

CIRCUIT THEORY AND NETWORKS (Backlog)

EE301

TIME ALLOTTED: 3HR

FULL MARKS: 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable

GROUP – A

(Multiple Choice Type Questions)

Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

	Marks	CO No
1(i) The equivalent resistance of the figure between x and y is	1	CO1
<ul style="list-style-type: none"> a) 30Ω b) 50Ω c) 60Ω d) 10Ω 		
1(ii) The Superposition Theorem is applicable to	1	CO1
<ul style="list-style-type: none"> a) Linear response only b) Linear and nonlinear response only c) Linear, Non-linear and time variant response only d) Linear, Non-linear and time invariant response only 		
1(iii) A R-C has a time constant given by	1	CO3
<ul style="list-style-type: none"> a) R/C b) C/R c) 1/(RC) d) RC 		
1(iv) Laplace transform analysis gives	1	CO2
<ul style="list-style-type: none"> a) Time domain response only b) Frequency domain response only c) Both A and B d) None of these 		
1(v) The value of the impulse function $\delta(t)$ at $t=0$ is	1	CO2
<ul style="list-style-type: none"> a) 0 b) ∞ c) 1 d) indeterminate. 		
1(vi) When a unit impulse voltage is applied to an inductor of 1H, the energy supplied by the source is	1	CO1
<ul style="list-style-type: none"> a) Infinite b) 0 c) 1/2J d) 1J 		

- | | | | |
|---------|--|---|-----|
| 1(vii) | The no of links for a graph having n nodes and b branches are
a) $b-n+1$
b) $n-b+1$
c) $b+n-1$
d) $b+n$ | 1 | CO5 |
| 1(viii) | A tie set matrix has 3 rows and 7 branches. The number of twigs is
a) 3
b) 5
c) 2
d) 4 | 1 | CO5 |
| 1(ix) | A two port network is reciprocal if and only if
a) $Z_{11}=Z_{22}$
b) $BC-AD= -1$
c) $A=D$
d) $Y_{11}=Y_{21}$ | 1 | CO4 |
| 1(x) | For maximum power to be transferred between the load and the source the condition is
a) $R_S > R_L$
b) $R_S = R_L$
c) $R_S < R_L$
d) None of these. | 1 | CO1 |
| 1(xi) | When a source is delivering max power to a load, the efficiency of the circuit
a) is always 50%
b) is always 75%
c) Depends on the circuit parameter
d) None of these | 1 | CO1 |
| 1(xii) | A cut-set schedule gives the relation between
a) Branch current and link current
b) Branch voltage and tree branch voltage
c) Branch voltage and link voltage
d) Branch and tree current | 1 | CO5 |


GROUP – B

(Short Answer Type Questions)


(Answer any *three* of the following)

3 x 5 = 15
Marks CO No
5 CO1

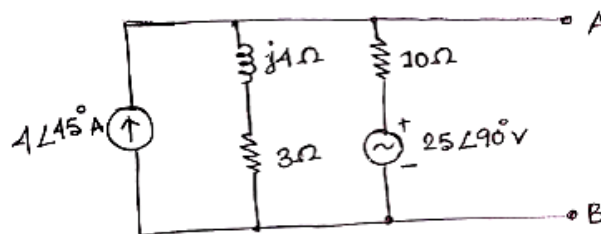
- 2 Find Norton's equivalent network across terminal A and B



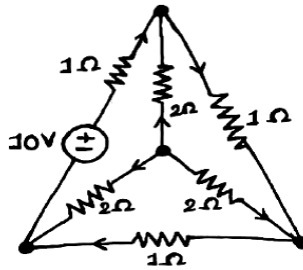
- 3 With reference to the figure draw the oriented graph and write down the Tie Set matrix.



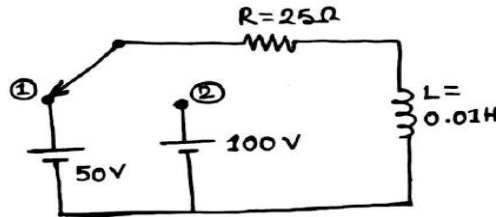- 4 The circuit in the figure was in steady state with switch in position 1. Find current $i(t)$ for $t > 0$ if the switch is moved from position 1 to 2 at $t = 0$. 5 CO2



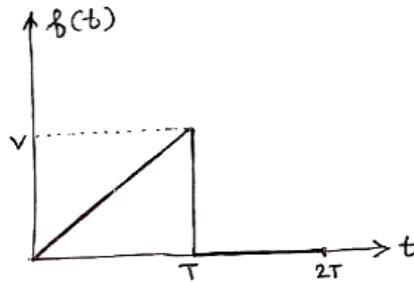- 6 Find the laplace transform of the waveform shown in figure. 5 CO3



- 6 What are ABCD parameters? Prove that $AD - BC = 1$ 5 CO4


GROUP – C

(Long Answer Type Questions)
(Answer any *three* of the following)


3 x 15 = 45

- 7.a) Find the Laplace transform of the periodic function shown in figure below:


Marks 5 **CO No** CO3

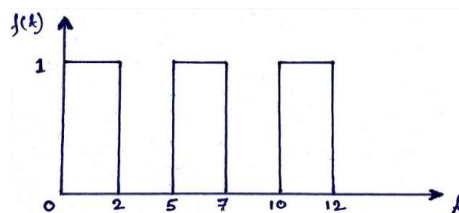

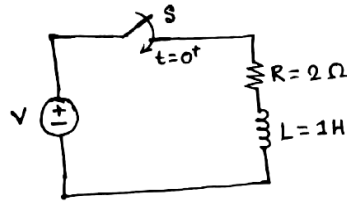
- 7.b) For an RL series circuit shown in figure, with no initial current in the inductor, a voltage $V = 4e^{-t}$ volts is applied at $t = 0$ sec. find the expression for the resulting current in the circuit for $t \geq 0$ using laplace transform method. 5 CO2



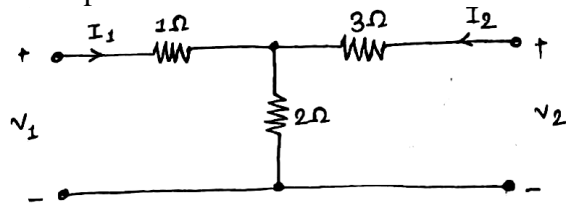- 7.c) Find the inverse Laplace transform of $F(s) = \frac{s^2 - 15s - 11}{(s+1)(s-2)^2}$ 5 CO2
- 8.a) Find Z-parameters in terms of Y-parameters of a two port network. 5 CO4
- 8.b) Deduce the condition for reciprocity and symmetry for the Z parameter of a two port network. 5 CO4
- 8.c) Find Y parameters for the network. Determine whether the network is symmetrical and reciprocal. 5 CO4



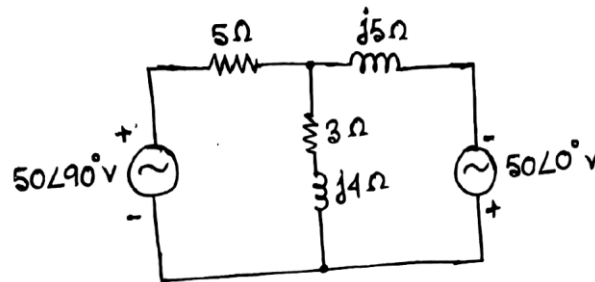- 9.a) State and explain Thevenin's theorem. 6 CO1
- 9.b) Find the current through $(3 + j4) \Omega$ impedance using Superposition theorem. 9 CO1



- 10.a) Design a first-order low pass filter with a cut-off frequency of 2 kHz and pass-band gain of 3. 7 CO3
- 10.b) What are the advantages of active filter over passive filter? 3 CO3
- 10.c) Draw and explain the characteristics of an ideal band-pass filter. 5 CO3
- 11.a) What is oriented graph of a network? Explain with a suitable example. 6 CO5
- 11.b) For the network shown in figure below write down the Tie set matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate loop currents. 9 CO5

