

**GURU NANAK INSTITUTE OF TECHNOLOGY**  
**An Autonomous Institute under MAKAUT**  
**2021**

**ANALOG ELECTRONIC CIRCUITS (Backlog)**  
**EC402**

**TIME ALLOTTED: 3 HOURS**

**FULL MARKS: 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable*

**GROUP – A**

**(Multiple Choice Type Questions)**

Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

|   | <b>Marks</b> | <b>CO No.</b> |
|---|--------------|---------------|
| 1. (i) Which of the following statement is true? Negative feedback in an amplifier          | 1            | CO3           |
| a) reduces gain   |              |               |
| b) increase frequency and phase distortion  |              |               |
| c) reduces bandwidth  |              |               |
| d) increases noise  |              |               |
| (ii) An instrumentation amplifier   | 1            | CO6           |
| a) is a differential amplifier  |              |               |
| b) has a gain less than 1   |              |               |
| c) has very high output impedance   |              |               |
| d) has low CMRR   |              |               |
| (iii) Which one of the following oscillator is used for the generation of high frequencies? | 1            | CO3           |
| a) R-C phase shift  |              |               |
| b) Blocking oscillator  |              |               |
| c) Wien bridge  |              |               |
| d) LC oscillator  |              |               |
| (iv) How can the duty cycle be changed for an astablemultivibrator?                         | 1            | CO3           |
| a) By adding another capacitor to the circuit   |              |               |
| b) By adding diodes to the circuit  |              |               |
| c) By adding an inductor to the circuit   |              |               |
| d) The duty cycle cannot be changed   |              |               |
| (v) In a logarithmic amplifier, the logarithmic effect of the input is obtained from        | 1            | CO4           |
| a) non-linear device, like diode or transistor  |              |               |
| b) negative feed-back   |              |               |
| c) the Op-Amp itself  |              |               |
| d) the inverting input terminal   |              |               |

- |  |   |     |
|--|---|-----|
| (vi) Operational amplifier are used to amplify   | 1 | CO6 |
| a) ac signal only  |   |     |
| b) dc signal only  |   |     |
| c) both ac and dc signal   |   |     |
| d) none of these   |   |     |
| (vii) Which power amplifier can deliver maximum load power?                            | 1 | CO5 |
| a) Class A   |   |     |
| b) Class AB  |   |     |
| c) Class B   |   |     |
| d) Class C   |   |     |
| (viii) The condition of oscillator   | 1 | CO3 |
| a) $A\beta=1$  |   |     |
| b) Feedback must be regenerated  |   |     |
| c) Phase angle must be zero  |   |     |
| d) All of these  |   |     |
| (ix) If RESET pin of 555 IC is made low, then output impedance of an OP-AMP is         | 1 | CO5 |
| a) output is high  |   |     |
| b) output is low   |   |     |
| c) IC will not work  |   |     |
| d) IC may be damaged   |   |     |
| (x) A comparator with a Schmitt trigger has  | 1 | CO6 |
| a) two trigger levels.   |   |     |
| b) a fast response.  |   |     |
| c) a slow response.  |   |     |
| d) one trigger level.  |   |     |
| (xi) The transformer-coupled amplifier provide   | 1 | CO1 |
| a) impedance matching  |   |     |
| b) maximum voltage gain  |   |     |
| c) maximum current gain  |   |     |
| d) large bandwidth   |   |     |
| (xii) For a wide range of oscillations in the audio range, the preferred oscillator is | 1 | CO3 |
| a) Hartley   |   |     |
| b) Phase-shift   |   |     |
| c) Colpitt   |   |     |
| d) Wine bridge   |   |     |

**GROUP – B**


**(Short Answer Type Questions)**

(Answer any *three* of the following)

**3 x 5 = 15**

- |   |              |               |
|---|--------------|---------------|
|   | <b>Marks</b> | <b>CO No.</b> |
| 2. a) Represent a comparative study for Astable & Monostable Multivibrator. | 3            | CO5           |

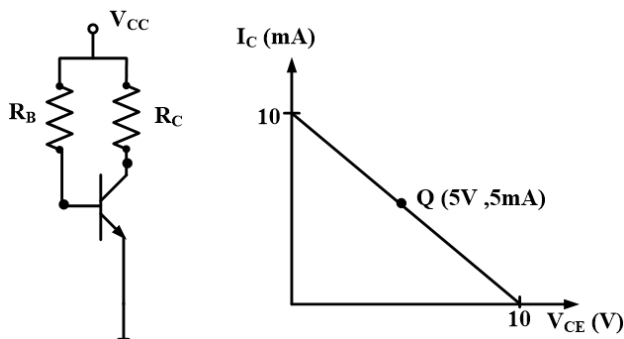- b) One circuit and its load line is shown in the Fig. Determine the value of  $V_{CC}$  and  $R_C$  of the circuit. 2 CO1




3. Draw a Wein-bridge oscillator circuit and derive an expression for the frequency of oscillation. 5 CO4
4. With a neat diagram, explain the principle of operation of an antilog amplifier. 5 CO4
5. Explain the operation of Transformer coupled class A power amplifier. 5 CO5
- 6 Draw and explain the Practical integrator circuit using Op-Amp. 5 CO6

### GROUP – C

**(Long Answer Type Questions)**  
(Answer any *three* of the following)

- |  | <b>Marks</b> | <b>3 x 15 = 45<br/>CO No.</b> |
|--|--------------|-------------------------------|
| 7. a) Draw the circuit diagram of an instrumentation amplifier using a transducer bridge. Explain its operation.   | 5            | CO6                           |
| b) With a neat diagram explain the concepts of “load line” and “Q point” of a transistor.  | 5            | CO1                           |
| c) Derive the condition for sustained oscillation and the expression for the frequency of oscillation of Colpitt’s Oscillator  | 5            | CO2                           |
| 8.a) Explain the operation of monostable multivibrator using 555 timer.  | 5            | CO5                           |
| b) Draw the circuit diagram of an astable multivibrator with 50% duty cycle output using 555 timer.  | 5            | CO4                           |
| c) Why bistable multivibrator is called a flip-flop multivibrator? Calculate the frequency and duty cycle of the output of an astable multivibrator using timer 555. Assume $R_1=25k\ \Omega$ , $R_2=50\ K\ \Omega$ and $C=0.1\ \mu F$ . | 5            | CO4                           |

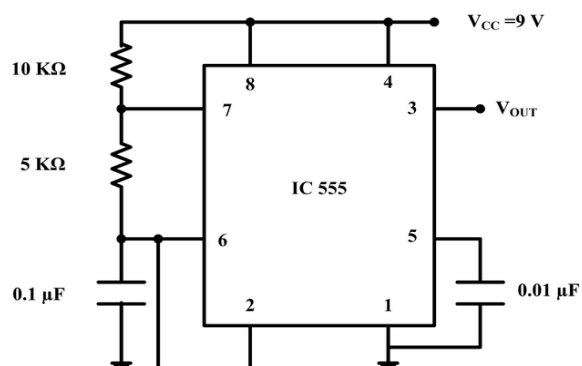- 9.a) What is the maximum voltage and minimum voltage across pin no. 2 of the following circuit ? 4 CO5



- b) In a Hartley oscillator,  $L_1 = 0.02 \text{ mH}$ , and  $C = 0.047 \mu\text{F}$ . When the frequency of the oscillator is  $100 \text{ KHz}$ , determine the value of  $L_2$ . Assume mutual inductance is negligible. 4 CO2
- c) Draw and explain the working of a push-pull class B power amplifier with proper circuit diagram. 7 CO3
- 10.a) Calculate the power conversion efficiency of it and maximum collector power dissipation. 7 CO3
- b) What is comparator? Explain non-inverting or inverting comparator? 5 CO6
- c) "Ideally the Bandwidth of Op-Amp is infinite"- What is the advantage? 3 CO2
11. Write short notes on any three of the following: 3X5=15
- Feedback topologies 5 CO3
  - Schmitt trigger circuit. 5 CO6
  - Hartley Oscillator 5 CO4
  - Structure of MOSFET with proper notification. 5 CO3
  - Precision rectifier 5 CO4