

GURU NANAK INSTITUTE OF TECHNOLOGY
An Autonomous Institute under MAKAUT
2021

DIGITAL ELECTRONICS & CIRCUITS (Backlog)
EC403

TIME ALLOTTED: 3 HOURS

FULL MARKS: 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable

GROUP – A

(Multiple Choice Type Questions)

Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

		Marks	CO No
1.	(i) The Boolean expression for a 3-input AND gate is _____ a) $X = AB$ b) $X = ABC$ c) $X = A + B + C$ d) $X = AB + C$	1	CO1
	(ii) The output of a NOR gate is HIGH if _____. a) all inputs are HIGH b) any input is HIGH c) any input is LOW d) all inputs are LOW	1	CO1
	(iii) When used with an IC, what does the term "QUAD" indicate? a) 2 circuits b) 4 circuits c) 6 circuits d) 8 circuits	1	CO1
	(iv) The NOR logic gate is the same as the operation of the _____ gate with an inverter connected to the output. a) OR b) AND c) NAND d) none of the above	1	CO1
	(v) Which of the following expressions is in the sum-of-products form? a) $(A + B)(C + D)$ b) $(AB)(CD)$ c) $AB(CD)$ d) $AB + CD$	1	CO1
	(vi) A decoder can be used as a demultiplexer by _____. a) tying all enable pins LOW b) tying all data-select lines LOW c) tying all data-select lines HIGH d) using the input lines for data selection and an enable line for data input	1	CO2

(vii)	How many data select lines are required for selecting eight inputs? a) 1 b) 2 c) 3 d) 4	1	CO2
(viii)	If both inputs of an S-R flip-flop are low, what will happen when the clock goes HIGH? a) An invalid state will exist b) No change will occur in the output c) The output will toggle. d) The output will reset.	1	CO3
(ix)	If an input is activated by a signal transition, it is _____. a) edge-triggered b) toggle triggered c) clock triggered d) noise triggered	1	CO3
(x)	Which is not characteristic of a shift register? a) Serial in/parallel in b) Serial in/parallel out c) Parallel in/serial out d) Parallel in/parallel out	1	CO3
(xi)	A Flip-Flop can Store _____ of information. a) 4 bit b) 1 byte c) 1 bit d) 8 bit	1	CO3
(xii)	A MOD 8 asynchronous counter needs _____ no of flip flops a) 2 b) 3 c) 4 d) 5	1	CO3

GROUP – B**(Short Answer Type Questions)**Answer any *three* from the following: **3×5=15**

		Marks	CO No
2.	Implement the following function using 8:1 MUX: $F(A,B,C,D) = \sum m(0,2,4,8,9)$	5	CO2
3.	(a) What is the difference between Half Adder and Full Adder?	1	CO2
	(b) Design a Full Adder circuit using 2 half adder.	4	CO2
4.	Simplify the following function using Karnaugh map and realize the expression using basic logic gates: $F(A,B,C,D) = \sum m(2,4,5,13,14) + \sum d(0,1,8,10)$	5	CO2
5.	Draw and explain the operation of a Master Slave flipflop.	5	CO3
6.	Describe Successive approximation ADC.	5	CO4

GROUP – C

(Long Answer Type Questions)

Answer any *three* from the following: $3 \times 15 = 45$

		Marks	CO No
7.	(a) Convert binary to decimal – (1011.101) ₂ = (?) ₁₀ Convert decimal to octal- (19.11) ₁₀ = (?) ₈ Convert hexadecimal to decimal (81.21) ₁₆ = (?) ₁₀	6	CO1
	(b) Simplify the expression using Boolean algebra $\bar{A}B + AB + \bar{A}\bar{B}$	4	CO1
	(c) Simplify the following expression using K Map for the 4 variables A, B, C, and D. $Y = m_1 + m_3 + m_5 + m_7 + m_8 + m_9 + m_{12} + m_{13}$	5	CO1
8.	(a) Explain De-Morgan's laws for simplification of Boolean expression	2	CO1
	(b) If $\bar{A}\bar{B} + \bar{A}B = C$, show that $A\bar{C} + \bar{A}C = B$	4	CO1
	(c) Simplify the Boolean function using K Map $F(A,B,C,D) = \sum m(1,3,7,11,15) + \sum d(0,2,5)$	5	CO1
	(d) Design a 8 X 1 Multiplexer using two 4 X 1 Multiplexer and a basic logic gate.	4	CO2
9.	(a) What is a decoder circuit? Construct a 5x32 decoder with four 3x8 decoders and a 2x4 decoder, show the block diagram only.	6	CO2
	(b) Why De Multiplexer is also known as Data Distributor? Implement the following Boolean function $F(A,B,C,D) = \sum (0,1,3,4,8,9,15)$ using a 8 : 1 Multiplexer	6	CO2
	(c) Draw and explain the State diagram for S-R flip flop	3	CO3
10.	(a) What is shift register? Mention the types of different shift registers.	3	CO3
	(b) Draw and explain a Serial In- Parallel Out (SIPO) left shift register.	5	CO3
	(c) Why asynchronous Counters are also known as Ripple Counters? Design a three-bit asynchronous binary up counter.	7	CO3
11.	Write short notes on any three of the following	3X5=15	
	(a) Parity Generator and Checker	5	CO2
	(b) Controlled Inverter	5	CO2
	(c) Excitation table for J-K flip flop	5	CO3
	(d) R-2R Digital-to-Analogue Converter	5	CO4
	(e) Ring Counter.	5	CO3