

GURU NANAK INSTITUTE OF TECHNOLOGY
An Autonomous Institute under MAKAUT
2021
DIGITAL ELECTRONICS
EE403

TIME ALLOTTED: 3HR

FULL MARKS:70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable***GROUP – A****(Multiple Choice Type Questions)**Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

		Marks	CO No.
1.	(i) The SR latch consists of _____ a) 1 input b) 3 inputs c) 2 inputs d) 4 inputs	1	CO4
	(ii) The SOP form of logical expression is most suitable for designing logic circuits using only a) XOR gate b) NOR gate c) OR gate d) AND gate	1	CO2
	(iii) The fastest logic gate family is a) CMOS b) ECL c) TTL d) RTL	1	CO4
	(iv) Race condition is avoided by a) J-K flip flop b) Master Slave flip flop c) D flip flop d) S-R flip flop	1	CO3
	(v) Gray code for $(1011)_2$ is a) 1000 b) 1101 c) 1110 d) None of these	1	CO1
	(vi) The SOP form of logical expression is most suitable for designing logic circuits using only a) XOR gates b) AND gates c) OR gates d) NAND gates	1	CO2
	(vii) D-flip flop can be used as a) Divider circuit b) Delay switch c) Differentiator d) None of these	1	CO3

- | | | | |
|--------|--|---|-----|
| (viii) | What type of register would shift a complete binary number in one bit at a time and shift all the stored bits out one bit at a time?
a) SIPO
b) PIPO
c) SISO
d) PISO | 1 | CO3 |
| (ix) | What type of register would shift a complete binary number in one bit at a time and shift all the stored bits out one bit at a time?
a) SIPO
b) PIPO
c) SISO
d) PISO | 1 | CO3 |
| (x) | In 4-to-1 multiplexer, if $S_1 = 1$ & $S_0 = 1$, then the output will be
a) Y_0
b) Y_1
c) Y_2
d) Y_3 | 1 | CO3 |
| (xi) | Excess code representation of decimal 984 is
a) 101110101101
b) 110010110111
c) 11010011010
d) 110111110111 | 1 | CO1 |
| (xii) | 2's complement of 1010111 is
a) 0101001
b) 0110110
c) 0101100
d) 0101101 | 1 | CO1 |

GROUP – B**(Short Answer Type Questions)**Answer any *three* from the following: $3 \times 5 = 15$

- | | | Marks | CO No. |
|----|---|--------------|---------------|
| 2. | Perform 2's complement subtraction of 010110-100101 | 5 | CO1 |
| 3. | Prove the following $(A+B)((AC)'+C)(B'+AC)'=A'B$ | 5 | CO2 |
| 4. | Write the logic gate diagram of 1*4 Demultiplexer. | 5 | CO3 |
| 5. | Perform the following operations:
(i) Convert Decimal 928 into Hexa decimal
(ii) Convert Hexa decimal 7AC .39 to the Binary
(iii) Subtract 1101 from 1111 using 2's complement | 5 | CO1,CO2 |
| 6. | Minimize the following boolean function- using Kmap
$F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 13, 15)$ | 5 | CO1,CO2 |

GROUP – C**(Long Answer Type Questions)**Answer any *three* from the following: $3 \times 15 = 45$

- | | | Marks | CO No. |
|--------|---|--------------|---------------|
| 7. (a) | Describe the bidirectional shift register with the help of circuit diagram. | 5 | CO3 |

(b) The figure below shows a full adder truth table

10

CO3

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(i) Write down the Boolean expressions for the sum bit and the carry output bit

(ii) Construct a full adder using combination of **AND**, **XOR** and **OR** gates.

- | | | | | |
|-----|-----|---|---|-----|
| 8. | (a) | What is difference between combinational and sequential circuits? | 6 | CO3 |
| | (b) | Simplify $f = A'BC' + AB'C + ABC$ using:
(a) Sum of minterms. (b) Maxterms | 9 | CO1 |
| 9. | (a) | Why parity checking is required? | 2 | CO3 |
| | (b) | Find the expression for segment “b”, “d” and “g” of a BCD 7 segment display. | 8 | CO3 |
| | (c) | Design a 4 bit up down counter. | 5 | CO3 |
| 10. | (a) | What do you mean by Race around condition of Flip-flop? | 3 | CO3 |
| | (b) | Design a Master Slave Flip-flop and discuss its operation. | 5 | CO3 |
| | (c) | Design a circuit to convert Binary to Grey code. | 7 | CO3 |
| 11. | (a) | Shift register | 5 | CO4 |
| | (b) | PROM | 5 | CO4 |
| | (c) | Demultiplexer | 5 | CO3 |
| | (d) | D/A & A/D Converters | 5 | CO4 |
| | (e) | TTL | 5 | CO4 |