

GURU NANAK INSTITUTE OF TECHNOLOGY
An Autonomous Institute under MAKAUT
2022
DIGITAL LOGIC AND ELECTRONICS
ESC302

TIME ALLOTTED: 3Hours

FULL MARKS:70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable***GROUP – A****(Multiple Choice Type Questions)**Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

- | | | | Marks | CO No |
|----|-------|---|-------|-------|
| 1. | (i) | What input should be given to “S” when SR flip – flop is converted to JK flip – flop?
a) K.Q
b) K.Q
c) J.Q
d) J.Q | 1 | CO3 |
| | (ii) | What value is to be considered for a “don’t care condition”?
a) 0
b) 1
c) Either 0 or 1
d) Any number except 0 and 1 | 1 | CO1 |
| | (iii) | Which of the following gives the correct number of multiplexers required to build a 32 x 1 multiplexer?
a) Two 16 x 1 mux
b) Three 8 x 1 mux
c) Two 8 x 1 mux
d) Three 16 x 1 mux | 1 | CO2 |
| | (iv) | What kind of operation occurs in a J – K flip flop when both inputs J and K are equal to 1?
a) Preset operation
b) Reset operation
c) Clear operation
d) Toggle operation | 1 | CO3 |
| | (v) | A priority encoder has four inputs I ₀ , I ₁ , I ₂ , and I ₃ where I ₃ has the highest priority and I ₀ has the least priority. If I ₂ = 1, what will be the output?
a) 00
b) 01
c) 10
d) 11 | 1 | CO2 |
| | (vi) | Total number of inputs in a half adder is _____
a) 2
b) 3
c) 4
d) 1 | 1 | CO2 |

- (vii) How much input and output needed for Demultiplexer? 1 CO3
 a) Many outputs to one input
 b) One input many outputs
 c) One input one output
 d) None of these
- (viii) If A and B are the inputs of a half adder, the carry is given by _____ 1 CO2
 a) A AND B
 b) A OR B
 c) A XOR B
 d) A EX-NOR B
- (ix) The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit parallel output shift register with an initial state 01110. After three clock pulses, the register contains _____ 1 CO3
 a) 01110
 b) 00001
 c) 00101
 d) 00110
- (x) The register is a type of _____ 1 CO3
 a) Sequential circuit
 b) Combinational circuit
 c) CPU
 d) Latches
- (xi) _____ is a digital circuit that is capable of storing only a single bit. 1 CO3
 a) Flip-flop
 b) NOR gate
 c) XOR gate
 d) Register
- (xii) The DeMorgan's Law would state that: 1 CO1
 a) $(AB)' = A + B$
 b) $(A+B)' = A' * B$
 c) $(AB)' = A' + B$
 d) $(AB)' = A' + B'$

GROUP – B**(Short Answer Type Questions)**Answer any *three* from the following

- | | | 3×5=15
Marks | CO No. |
|----|--|-----------------|--------|
| 2. | Design a 4-bit bidirectional shift register. | 5 | CO3 |
| 3. | Obtain the (i) canonical SOP and (ii) canonical POS for the following:
$F(A,B,C) = A + B'C$ | 5 | CO1 |
| 4. | Design the circuit of 16: 1 MUX by using 8: 1 MUX only. | 5 | CO3 |
| 5. | What is K-map? Solve the expression using K-map and find SOP.
$F(A, B, C, D) = \sum(7, 13, 14, 15)$ | 5 | CO1 |

6. Obtain the simplified function in sum of products (SOP) expression from the following truth table 5 CO1

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

GROUP – C

(Long Answer Type Questions)

Answer any *three* from the following

3×15=45

- | | | Marks | CO No. |
|-----|---|-------|--------|
| 7. | (a) Design a 2-bit comparator circuit with suitable truth table and diagram. | 5 | CO2 |
| | (b) Explain the logic of a 4-bits carry look-ahead adder with suitable diagram. | 5 | CO2 |
| | (c) Design the circuit of 3:8 decoder and verify its truth table. | 5 | CO2 |
| 8. | (a) Describe JK Flip-Flop with truth table and characteristics table. | 5 | CO3 |
| | (b) Construct a D flip-flop using S-R flip-flop. Explain its characteristic table and excitation table. | 5 | CO3 |
| | (c) Minimize the following expression using K-map
$Y(A, B, C, D) = \sum m(1, 2, 3, 5, 6, 11, 12) + D(7, 8, 10, 14)$ | 5 | CO1 |
| 9. | (a) With a circuit diagram, explain the operation of 4 bits Johnson counter implemented using D flip-flop. | 5 | CO3 |
| | (b) Explain 4X2 Encoder with truth table and diagram. | 5 | CO3 |
| | (c) Differentiate between Programmable logic Array and Programmable Array logic. | 5 | CO4 |
| 10. | (a) What do you mean by excitation table? | 2 | CO3 |
| | (b) Draw the clocked Master-Slave J-K flip-flop configuration and explain how it removes race-around condition in J-K flip-flops. | 7 | CO3 |
| | (c) Design Mod 3 synchronous counter. | 6 | CO2 |
| 11. | (a) What is the application of shift register? | 2 | CO3 |
| | (b) Design the circuit of PISO and explain its operation. | 7 | CO3 |
| | (c) Design the circuit of BCD to 7-Segment display. | 6 | CO2 |