


GURU NANAK INSTITUTE OF TECHNOLOGY
An Autonomous Institute under MAKAUT
2022
POWER ELECTRONICS
EE402

TIME ALLOTTED: 3 Hrs

FULL MARKS: 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable***GROUP – A****(Multiple Choice Type Questions)**Answer any **ten** from the following, choosing the correct alternative of each question: **10×1=10**

1. (i) In the positive half cycle from $\omega t = 0$ to π

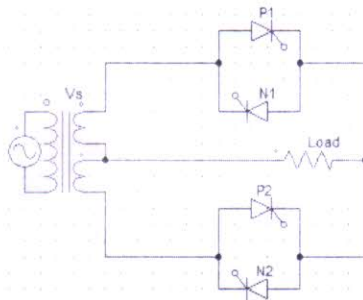Marks
1CO No.
CO1

- a) P1 and P2 are forward biased
 b) N1 and P2 are forward biased
 c) P1 and N2 are forward biased
 d) None of the mentioned

- (ii) The forward break over voltage is the

1

CO4

- a) anode-cathode voltage at which conduction starts with gate signal applied
 b) anode-cathode voltage at which conduction starts with no gate signal applied
 c) gate voltage at which conduction starts with no anode-cathode voltage
 d) gate voltage at which conduction starts with anode-cathode voltage applied

- (iii) The average value of voltage of a single-phase ac voltage controller is given by

1

CO2

- a) $\frac{\sqrt{2}V}{\pi}(1 + \cos \alpha)$
 b) $\frac{\sqrt{2}V}{2\pi}(1 + \cos \alpha)$
 c) $\frac{\sqrt{2}V}{\pi} \cos \alpha$
 d) $\frac{V}{\pi} \cos \alpha$

- | | | | |
|--------|---|---|-----|
| (iv) | Find the output voltage expression for a step down chopper with V_s as the input voltage and α as the duty cycle. | 1 | CO1 |
| | a) $V_o = V_s/\alpha$ | | |
| | b) $V_o = V_s \times \alpha$ | | |
| | c) $V_o = V_s^2/\alpha$ | | |
| | d) $V_o = 2V_s/\alpha\pi$ | | |
| (v) | If a step down chopper operates in the continuous conduction mode, the ripple in load current is maximum when duty cycle is | 1 | CO2 |
| | a) 0.25 | | |
| | b) 0.5 | | |
| | c) 0.75 | | |
| | d) 1.0 | | |
| (vi) | A freewheeling diode across inductive load of a phase-controlled converter will provide | 1 | CO3 |
| | a) quick turn-on of SCR | | |
| | b) slow turn-off of SCR | | |
| | c) reduced utilization factor of transformer | | |
| | d) improved power factor | | |
| (vii) | If input DC voltage is constant, the output voltage of a single-phase bridge inverter can be controlled by | 1 | CO2 |
| | a) Pulse width modulation | | |
| | b) Changing the switching frequency | | |
| | c) Pulse amplitude modulation | | |
| | d) All of these | | |
| (viii) | Each diode of a 3-phase half-wave diode rectifier conducts for | 1 | CO2 |
| | a) 60° | | |
| | b) 120° | | |
| | c) 180° | | |
| | d) 90° | | |
| (ix) | An IGBT has three terminals called | 1 | CO1 |
| | a) collector, emitter, base | | |
| | b) drain, source, base | | |
| | c) drain, source, gate | | |
| | d) collector, emitter, gate | | |

- (x) The effective input resistance R_i of a step down chopper is 1 CO1
- $\frac{R}{D}$
 - RD
 - $\frac{R}{1-D}$
 - $(1-D)R$
- (xi) When a Three Phase Voltage Source Inverter operates in 180 degree conduction mode, the rms line to line voltage is ----- 1 CO1
- $V_{L(rms)} = \frac{\sqrt{2}}{\sqrt{3}} V$
 - $V_{L(rms)} = \frac{\sqrt{2}}{3} V$
 - $V_{L(rms)} = \frac{1}{\sqrt{3}} V$
 - $V_{L(rms)} = V$
- (xii) The output voltage waveform of a three phasesquare wave inverter contains 1 CO2
- only odd harmonics
 - both odd and even harmonics
 - only even harmonics
 - only triplen harmonics


GROUP – B**(Short Answer Type Questions)**(Answer any *three* of the following)**3 x 5 = 15**

- | | Marks | CO No. |
|--|-------|--------|
| 2. Explain the two transistor analogy of thyristor
Derive an equation for anode current.
State the condition for turn on. | 5 | CO1 |
| 3. Why are freewheeling diode connected in rectifier circuits to copeup with R-L load? (Give waveforms). | 5 | CO2 |
| 4.(a) Describe the different modes of operation using static V-I characteristics of thyristor. | 3 | CO2 |
| (b) Define Holding Current and Latching current. | 2 | CO2 |
| 5. What are the different types of inverters ? Write difference between VSI and CSI. | 5 | CO2 |
| 6. A three-phase inverter is supplied from a 580 V source. For a star connected resistive load of 20 Ω per phase, for 120° conduction, determine the
i) r.m.s. value of phase voltage
ii) r.m.s. value of switch current. | 5 | CO2 |

GROUP – C
(Long Answer Type Questions)
 (Answer any three of the following)

3 x 15 = 45
 Marks CO No.

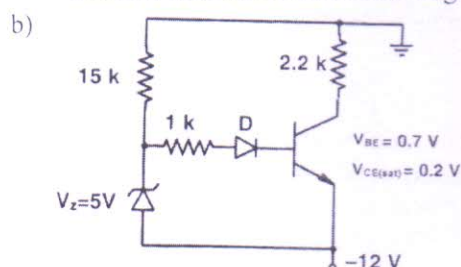- 7.a) Explain with the help of circuit diagram, the principle of operation of step-up chopper. 6 CO2
- b) For a type A chopper, dc source voltage = 230 V, load resistance = 10 Ω . Take a drop of 2 V across chopper when it is on. For a duty cycle of 0.4, calculate
 i) average and rms values of output voltage
 ii) Chopper efficiency. 6 CO2
- c) What is the effect of source inductance on the performance of a single phase fully controlled converter. 2 CO3
8. a) Why are freewheeling diodes used in rectifier circuit? 6 CO3
- b) A chopper circuit is operating on Time Ratio Control (TRC) principle at a frequency of 2kHz on a 220 V d.c supply. If the load voltage is 170 V, compute the conduction and blocking period of thyristor in each cycle. 6 CO2
- c) Explain the operation of 3-phase six pulse bridge rectifier circuit when $\alpha=30^\circ$ deg. 3 CO3
9. a) Explain the working principle of a single phase a.c voltage regulator feeding a resistive load with neat circuit diagram. 7 CO2



- 5 CO3
- The transistor used in the circuit shown below has a β of 30 and I_{CBO} is negligible. If the forward voltage drop of diode is 0.7V, then What amount of current through the collector?
- c) A single phase full bridge inverter has RLC load of $R = 4 \Omega$, $L = 35 \text{ mH}$, $C = 155 \mu\text{F}$. The dc input voltage is 230 V and the output frequency is 50 Hz. Find 2 CO1
- 10.a) Explain the working of a full bridge three phase inverter with resistive load in 180 degree conduction? 8 CO2
- Draw the circuit diagrams and phase and line output voltages.
- b) What is the Pulse Width modulated Inverters? What are the different types of PWM Techniques are used in Inverters? 2 CO2
- c) Explain the following performance parameters: 5 CO2
- (a) Total Harmonic Distortion
- (b) Distortion Factor
11. Write short note on (any three) 3X5=15
- a) Different modes of operation using static V-I characteristics of thyristor. 5 CO1
- b) GTO 5 CO2
- c) Class C Chopper 5 CO2
- d) Effect of Source Inductor in Single Phase Rectifier 5 CO3
- e) Single Phase Semi Control rectifier 5 CO3