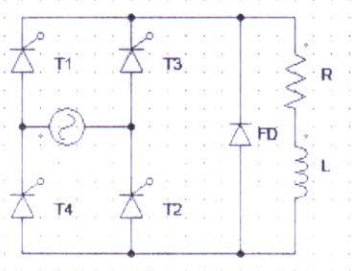
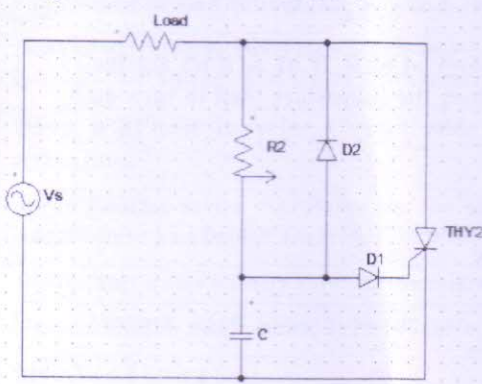
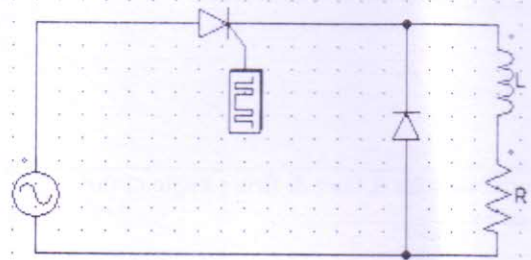


GURU NANAK INSTITUTE OF TECHNOLOGY			
An Autonomous Institute under MAKAUT			
2022			
POWER ELECTRONICS			
EI 604A			
TIME ALLOTTED: 3HR		FULL MARKS:70	
<i>The figures in the margin indicate full marks.</i>			
<i>Candidates are required to give their answers in their own words as far as practicable</i>			
GROUP – A			
(Multiple Choice Type Questions)			
Answer any ten from the following, choosing the correct alternative of each question: 10×1=10			
1.		Marks	CO No.
(i)	Consider the two-transistor analogy of SCR, if α_1 & if α_2 are the common-base current gains of both the transistors then to turn-on the device a) $\alpha_1 + \alpha_2$ should approach zero b) $\alpha_1 \times \alpha_2$ should approach unity c) $\alpha_1 - \alpha_2$ should approach zero d) $\alpha_1 + \alpha_2$ should approach unity	1	CO1
(ii)	For the below shown circuit has dis-continuous load current waveform.  Each thyristor pair conducts for a) π radians b) 2π radians c) $< \pi$ radians d) $> \pi$ radians	1	CO2
(iii)	The latching current is _____ than the holding current a) lower b) higher c) same as d) negative of	1	CO1
(iv)	For a single-phase thyristor circuit with R load & firing angle α , the conduction angle can be given by a) $\pi + \alpha$ b) $2\pi + \alpha$ c) $\pi - \alpha$ d) α	1	CO2

(v)	<p>The type of commutation in which the pulse to turn off the SCR is obtained by separate voltage source is</p> <p>a) class B commutation b) class C commutation c) class D commutation d) class E commutation</p>	1	CO1
(vi)	<p>A chopper may be thought as a</p> <p>a) Inverter with DC input b) DC equivalent of an AC transformer c) Diode rectifier d) DC equivalent of an induction motor</p>	1	CO3
(vii)	<p>The figure shown below is that of a</p>  <p>a) R firing circuit b) RC half-wave firing circuit c) RC full-wave firing circuit d) UJT triggering circuit</p>	1	CO2
(viii)	<p>In a 3-phase full converter using six SCRs, gating circuit must provide</p> <p>a) one firing pulse every 30° b) one firing pulse every 90° c) one firing pulse every 60° d) three firing pulses per cycle</p>	1	CO2
(ix)	<p>In the below given circuit, the FD (Freewheeling diode) is forward biased at $\omega t =$</p>  <p>a) 0 b) α</p>	1	CO1

		c) π d) 2π		
(x)		A cycloconverter is a _____ a) one stage power converter b) one stage voltage converter c) one stage frequency converter d) none of the mentioned	1	CO3
(xi)		In a single-phase half-wave thyristor circuit with R load & $V_s = V_m \sin \omega t$, the maximum value of the load current can be given by a) $2V_m/R$ b) V_s/R c) $V_m/2$ d) $V_s/2$	1	CO2
(xii)		The dv/dt protection is provided in order to a) limit the power loss b) reduce the junction temperature c) avoid accidental turn-on of the device d) avoiding sudden large voltage across the load	1	CO1

GROUP – B
(Short Answer Type Questions)

Answer any *three* from the following: $3 \times 5 = 15$

			Marks	CO No.
2.	(a)	What is Holding current and Latching current?	3	CO1
	(b)	Draw the SCR Characteristics and point out these two parameters	2	CO1
3.		With the help of circuit, diagram and waveform explain the operation of UJT triggering circuit for one Thyristor.	5	CO2
4.		Describe the basic behavior of Thyristor using a two- transistor model and find its Anode current expression.	5	CO1
5.		Draw the circuit and derive the expression for output voltage of a single-phase bridge converter.	5	CO3
6.		Draw the circuit of step-up chopper and explain its working.	5	CO3

GROUP – C
(Long Answer Type Questions)

Answer any *three* from the following: $3 \times 15 = 45$

			Marks	CO No.
7.	(a)	What is reverse recovery period of power diode? What is snubber circuit? Explain it with the proper circuit diagram.	7	CO1
	(b)	Describe the V-I characteristics of TRIAC and modes of operation.	4	CO1
	(c)	Explain the operation of IGBT with the representation of its schematic diagram.	4	CO1
8.	(a)	Draw the circuit of buck boost converter and explain its working.	4	CO3

	(b)	For a type A chopper, dc source voltage is 230 V, load resistance 10 Ω , drop across the switch is 2V and duty cycle 0.4. Calculate average and RMS value of output voltage and chopper efficiency.	6	CO3
	(c)	Describe the working of a three-phase voltage source inverter with an appropriate circuit diagram.	5	CO2
9.	(a)	With the help of circuit diagram explain the operation of single-phase semi converter with RL load. Draw the waveform of input voltage, output voltage, load current and voltage across the Thyristor.	5	CO2
	(b)	With the help of circuit diagram, explain the working of three-phase semi controlled converter.	4	CO2
	(c)	A single-phase half-controlled rectifier supplies a resistive load draws an average current of 1.6A. If the converter is operated from a 240V, 50 Hz supply and if the average value of the Output voltage is 81V, Calculate The firing angle, Load Resistance, the r.m.s. value of load voltage, DC power & the ripple factor.	6	CO2
10.	(a)	Draw a half Bridge Inverter Circuit and Explain its working and draw its O/P voltage and Current waveform.	5	CO2
	(b)	Draw a 3Phase inverter Circuit and explain its modes of operation.	7	CO3
	(c)	Write Fourier series expression for the output voltage from the single-phase half bridge Inverter Circuit.	3	CO3
11.	(a)	Write short notes on Any three of the following: - Single-phase to single-phase cycloconverter	5	CO3
	(b)	Induction heating	5	CO3
	(c)	SMPS	5	CO4
	(d)	IPM	5	CO4
	(e)	Buck Converter	5	CO4